

CS 230 Project IITB RISC Report

Adish Shah, Akshay Padakanti, Swayam Chube and Vivek Veer

3rd April, 2022

Contents

1	Instructions	2
1.1	Finite State Machine	3
1.1.1	Instructions : ADD,ADC,ADZ,NDU,NDC,NDZ	3
1.1.2	ADI	4
1.1.3	LHI	5
1.1.4	LW	6
1.1.5	SW	6
1.1.6	LM	7
1.1.7	SM	8
1.1.8	BEQ	9
1.1.9	JAL	10
1.1.10	JLR	11
1.1.11	JRI	12

1 Instructions

The basic structure of all the instructions is as follows :

R Type : | op-code (4 bits) | RegA (3) | Reg B (3) | Reg C (3) | Unused(1) | Condition (2)

I Type : | op-code (4 bits) | RegA (3) | Reg B (3)
Immediate (8) |

J Type : | op-code (4 bits) | RegA (3)
Immediate (9 bit signed) |

The implementation is as follows :

1. Sending the Program Counter to memory and fetching the instruction and incrementing PC
2. Decode the instructions and read the registers. In case of Jump and BEQ, we can also calculate the target address by adding immediate to PC.
3. Then, operations are performed on the read values using the ALU. Also immediate is added to the base address in this step.
4. In case of load/store, memory is read/written to in this step.
5. The result is stored back in the Register File.

1.1 Finite State Machine

1.1.1 Instructions : ADD, ADC, ADZ, NDU, NDC, NDZ

States :

PC \rightarrow Mem_A	Mem-Read
Mem_D \rightarrow IR	IR-Write

Table 1: S0 : Read Instruction

PC \rightarrow ALU_A	PC-Write
+1 \rightarrow ALU_B	ALU_ADD
ALU_C \rightarrow PC	

Table 2: S00 : Increment PC

IR ₁₁₋₉ \rightarrow RF-A1	t1-Write
IR ₈₋₆ \rightarrow RF-A2	t2-write
RF-D1 \rightarrow t1	
RF-D2 \rightarrow t2	


Table 3: S1 : Read Registers

t1 \rightarrow ALU_A	t3-Write
t2 \rightarrow ALU_B	ALU-Operation
ALU_Carry \rightarrow C	ALU_C \rightarrow t3
ALU_Zero \rightarrow Z	

Table 4: S2 : Perform Operation

t3 \rightarrow RF-D3	t1-Write
IR ₅₋₃ \rightarrow RF-A3	

Table 5: S3: Write to register File

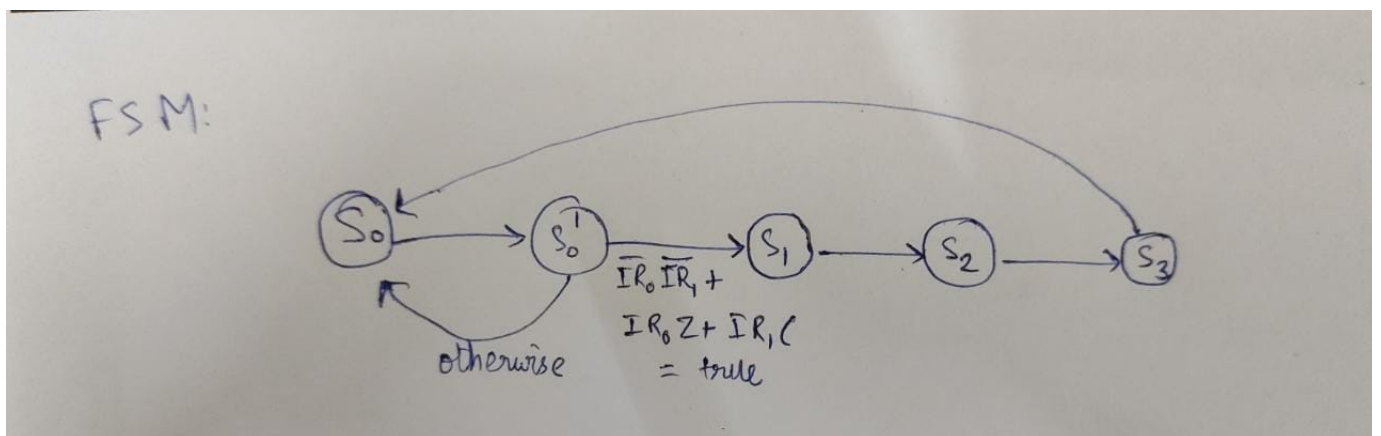

The condition on $S_0 \rightarrow S_1$ is to ensure that the addition is done only if conditions for instruction are met. For example, ADC needs C to be set. So, if the command is ADC (identified by $IR_1 = 1$), we need to make sure $C = 1$. This is done using the given formula. The condition is written in compact here, we can easily use a decoder to do the transition (use 4 bit decoder with inputs being ir_0, ir_1, c, z).

1.1.2 ADI


States :

$IR_{11-9} \rightarrow RF-A1$	t1-Write
$IR_{5-0} \rightarrow SE_6$	t2-write
$RF-D1 \rightarrow t1$	
$SE_6 \rightarrow t2$	

Table 6: S_4 : Read Register and immediate value

$t3 \rightarrow RF-D3$	RF-Write
$IR_{8-6} \rightarrow RF-A3$	

Table 7: S_5 : Write to register File

 

1.1.3 LHI


States :

$IR_{8-0} \rightarrow SE_9$	7 bit shifter t3-Write
$SE_9 \rightarrow ALU_A$	
$ALU_C \rightarrow t3$	

Table 8: S6

$t3 \rightarrow RF-D3$	RF-Write
$IR_{11-9} \rightarrow RF-A3$	

Table 9: S7: Write to RF

 

1.1.4 LW


States :

$IR_{8-6} \rightarrow RF-A2$	t1-Write
$IR_{5-0} \rightarrow SE_6$	t2-write
$RF-D2 \rightarrow t2$	
$SE_6 \rightarrow t1$	

Table 10: S8 : Calculating Address

$t3 \rightarrow Mem_A$	Mem-Read
$Mem_D \rightarrow RF-D3$	RF-Write
$IR_{11-9} \rightarrow RF-A3$	


Table 11: S9: Load

 **1.1.5 SW**

States :

$t3 \rightarrow Mem_A$	Mem-write
$IR_{11-9} \rightarrow RF-A$	
$RF-D \rightarrow Mem_D$	

Table 12: S10: writing to memory

 

1.1.6 LM

States :

$IR_{11-9} \rightarrow RF-A1$	t1-Write
$IR_{8-0} \rightarrow SE_9$	t2-write
$SE_9 \rightarrow t3$	t3-write
$RF-D1 \rightarrow t1$	
$000 \rightarrow t2$	

Table 13: S11 : Read memory address, immediate and initialise counter

if (immediate bit of register is set)	
$t1 \rightarrow Mem_A$	Mem-Read
$Mem_D \rightarrow RF-D3$	RF-Write
$t2 \rightarrow RF-A3$	


Table 14: S12 : read memory and write to RF

$t1 \rightarrow ALU_A$	t1-Write
$+1 \rightarrow ALU_B$	ALU_ADD
$ALU_C \rightarrow t1$	

Table 15: S13 : Increase memory address

$t2 \rightarrow ALU_A$	t2-Write
$+1 \rightarrow ALU_B$	ALU_ADD
$ALU_C \rightarrow t2$	


Table 16: S14 : Increase counter

 

1.1.7 SM

if (immediate bit of register is set)		Mem-write
$t_2 \rightarrow \text{RF-A1}$		
$\text{RF-D1} \rightarrow \text{Mem_D}$		
$t_1 \rightarrow \text{Mem_A}$		

Table 17: S15: writing to memory

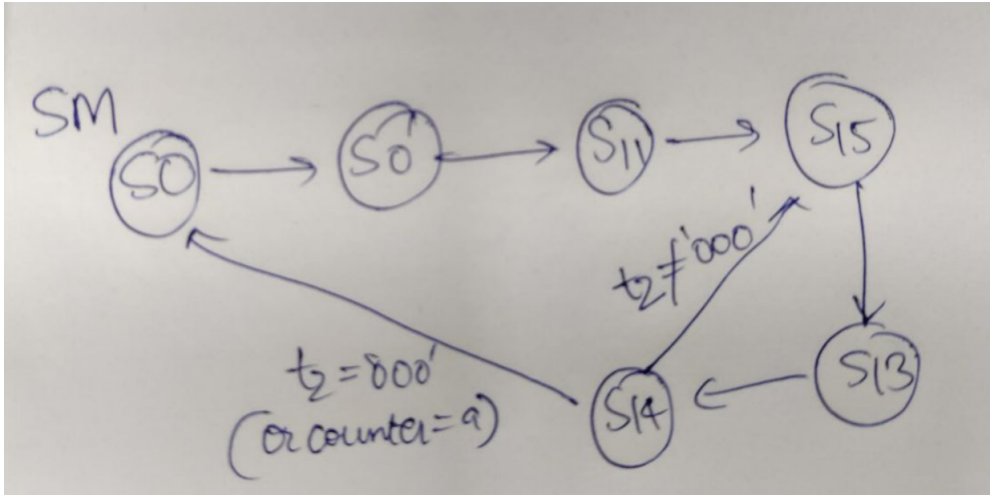

1.1.8 BEQ


States :

$t1 \rightarrow \text{ALU_A}$	$t3\text{-write}$
$t2 \rightarrow \text{ALU_B}$	ALU_SUB
$\text{ALU_C} \rightarrow t3$	

Table 18: S16 : Increment PC

$\text{PC} \rightarrow \text{ALU_A}$	PC-Write
$\text{IR}_{5-0} \rightarrow \text{SE}_6$	ALU_ADD
$\text{SE}_6 \rightarrow \text{ALU_B}$	
$\text{ALU_C} \rightarrow \text{PC}$	

Table 19: S17 : Increment PC

 

1.1.9 JAL


States :

$IR_{11-9} \rightarrow RF-A3$	RF-Write
$PC \rightarrow RF-D3$	

Table 20: S18: Store PC

$PC \rightarrow ALU_A$	PC-Write ALU_ADD
$IR_{8-0} \rightarrow SE_9$	
$SE_9 \rightarrow ALU_B$	
$ALU_C \rightarrow PC$	

Table 21: S19 : Increment PC

 


1.1.10 JLR

States :

$IR_{8-6} \rightarrow RF-A1$		PC-Write
$RF-D1 \rightarrow PC$		

Table 22: S20: Store PC

 

1.1.11 JRI

States :

$IR_{11-9} \rightarrow RF_A1$	RF-Write
$RF_D1 \rightarrow t3$	t3-Write

Table 23: S21: Store PC

$t3 \rightarrow ALU_A$	ALU-ADD
if $iR(8) == 0$	
"000000" & $IR_{8-0} \rightarrow ALU_B$	PC-Write
else	
"111111" & $IR_{8-0} \rightarrow ALU_B$	
$ALU_C \rightarrow PC$	

Table 24: S22: Store PC

